

Reducing current consumption at 32 kHz with ST62

INTRODUCTION

In many cases a 32kHz crystal is chosen for the oscillator of the ST62 microcontroller in order to achieve the minimum current consumption in the application.

This note provides a technique for minimising the current consumption when using a crystal oscillator at this frequency.

The note should be read in conjunction with Application Note AN670 - Oscillator Selection for the ST62.

1 CIRCUIT MODIFICATION

A standard oscillator circuit is shown in Figure 1. This circuit is suitable for higher frequency oscillations up to the maximum oscillation frequency of the ST62.

The current consumption of the oscillator of the ST62 can be reduced effectively when a resistor is added in the circuit as shown in Figure 2.

Figure 1. Standard Circuit.


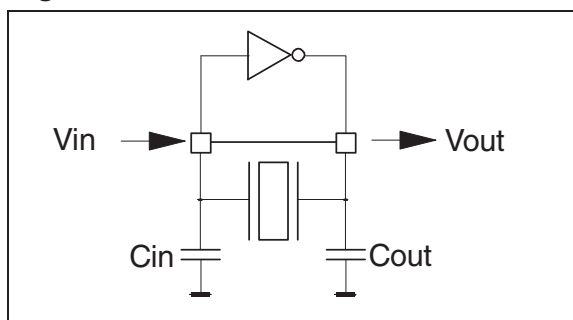


Figure 2. Modified Circuit.

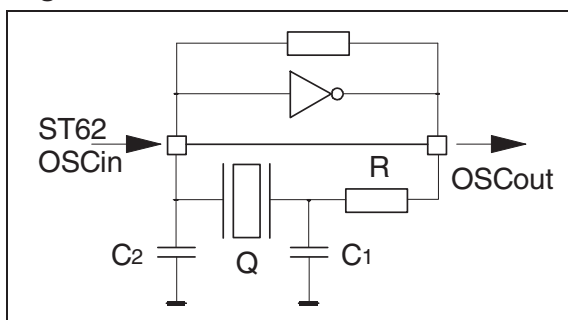

The Resistor (R) limits the power dissipation through the crystal, resulting in a lower load for the inverter circuit and a minimum power consumption.

Note that the resistor adds a phase shift to the Capacitor and oscillator network. This shift must not be excessive such that it affects the loop functionality.

Recommended values are:

R = 330K

C1 = 33 pF

C2 = 33 pF

Q = 32.8kHz crystal

2 RESULTS

The current consumption in WAIT mode measures the oscillator consumption as long as there is no additional consumption in the I/O pins with their associated external circuits.

The following table indicates the typical potential current saving in the WAIT mode of the ST62E2x microcontroller at a temperature of 25 C.

Typical current saving (32kHz crystal)

	Standard oscillator	Modified oscillator
5V	900 μ A	450 μ A
3V	50 μ A	35 μ A

The oscillator start-up time is also increased and ranges from 300 to 500 ms. This is due to the R, C1 time constant and the normal start-up time of the 32kHz crystal (typically around 250ms). The use of this additional resistor is made possible by the high gain of the inverter in the ST62 oscillator circuit when working at 32kHz and the characteristics of a standard 32kHz crystal.

Revision history

Date	Revision	Description of changes
February 1994	1	Initial release
05-Aug-2008	2	Logo and disclaimer modified

Please Read Carefully:

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at any time, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

UNLESS EXPRESSLY APPROVED IN WRITING BY AN AUTHORIZED ST REPRESENTATIVE, ST PRODUCTS ARE NOT RECOMMENDED, AUTHORIZED OR WARRANTED FOR USE IN MILITARY, AIR CRAFT, SPACE, LIFE SAVING, OR LIFE SUSTAINING APPLICATIONS, NOR IN PRODUCTS OR SYSTEMS WHERE FAILURE OR MALFUNCTION MAY RESULT IN PERSONAL INJURY, DEATH, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE. ST PRODUCTS WHICH ARE NOT SPECIFIED AS "AUTOMOTIVE GRADE" MAY ONLY BE USED IN AUTOMOTIVE APPLICATIONS AT USER'S OWN RISK.

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2008 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

www.st.com